


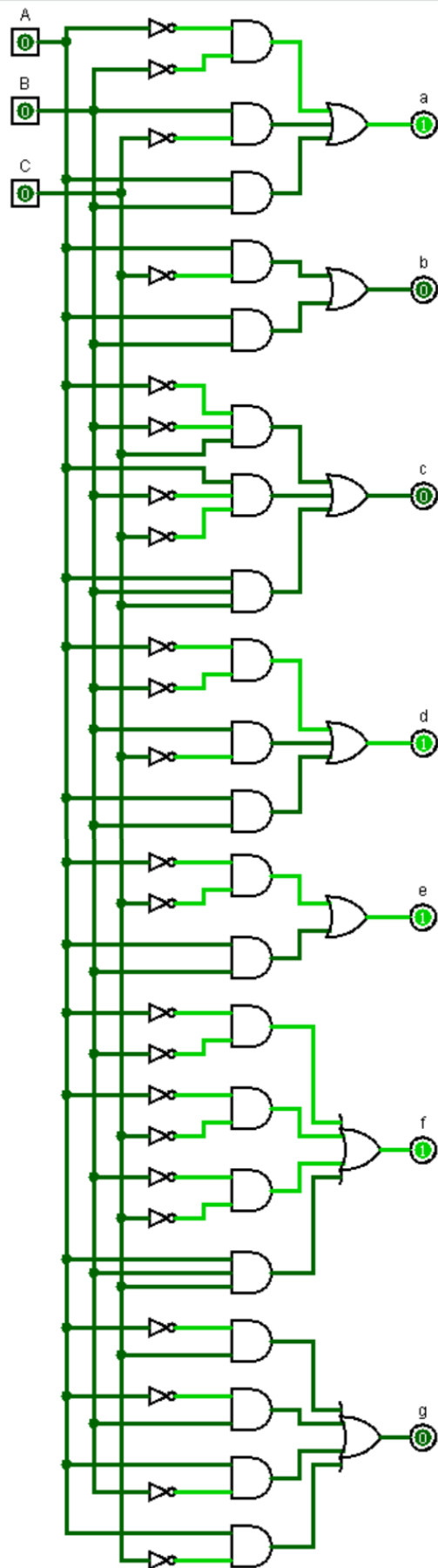
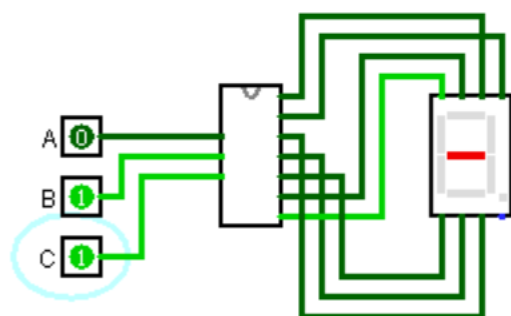
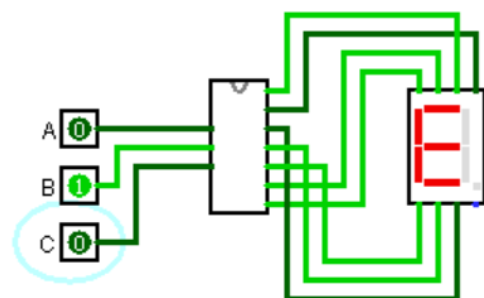
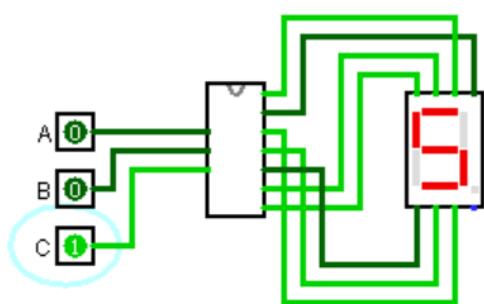
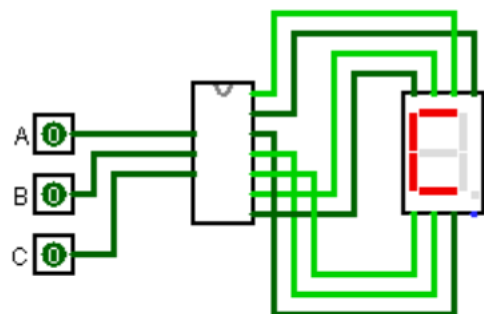
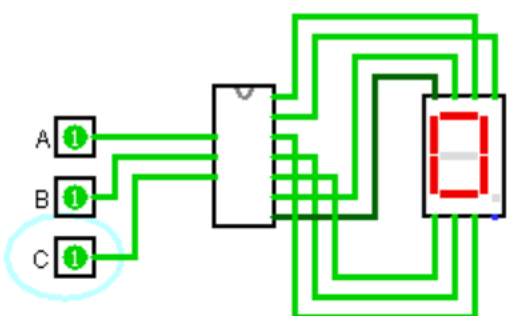


## Using SOP Circuit

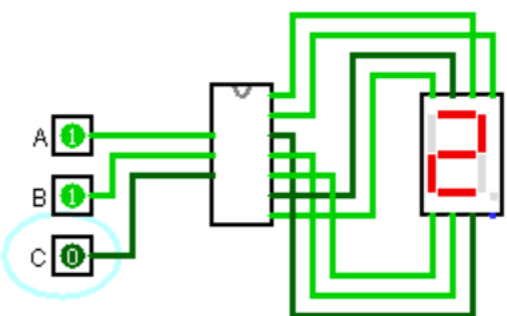


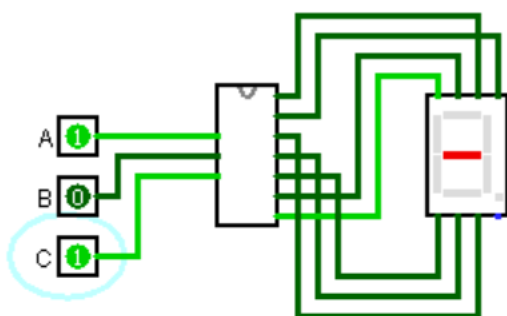SOP is done by Shadman Sakib Ayan.  
ID:2014172642











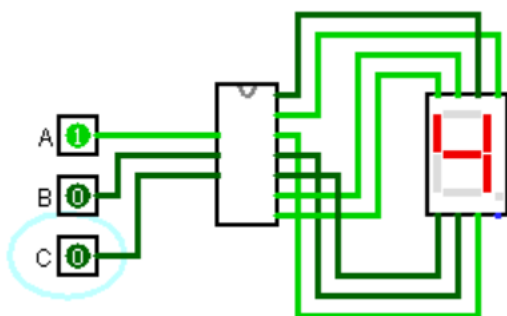


## Using POS Circuit

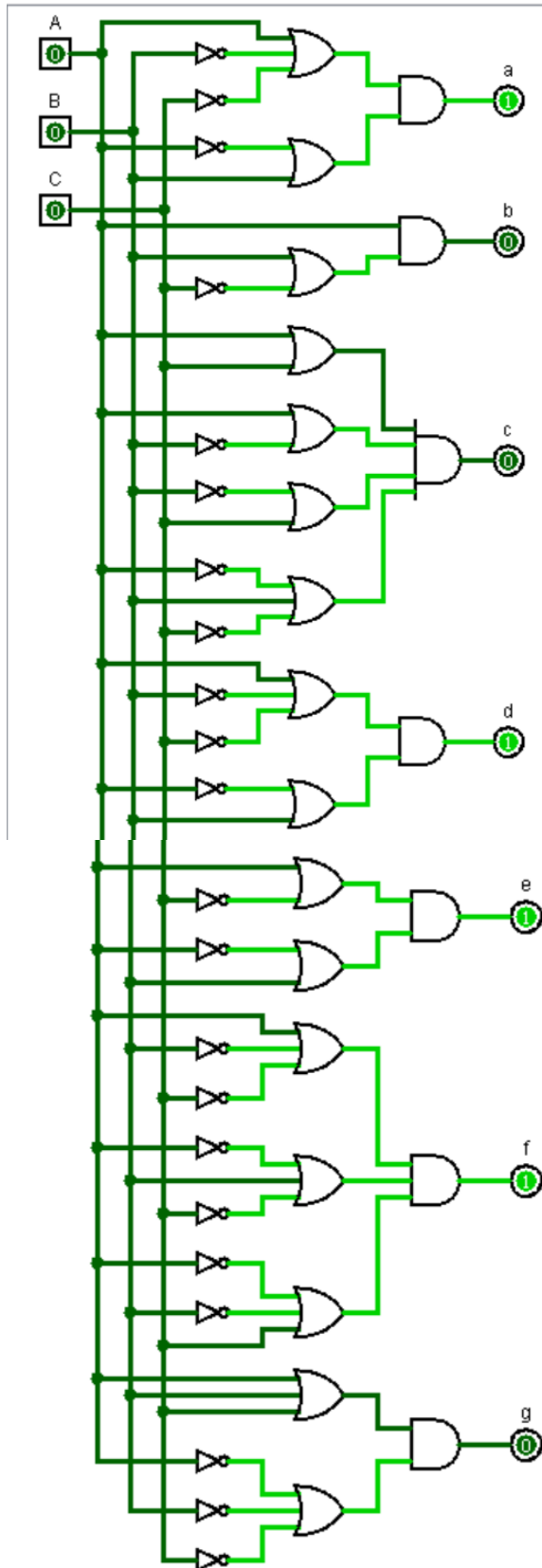

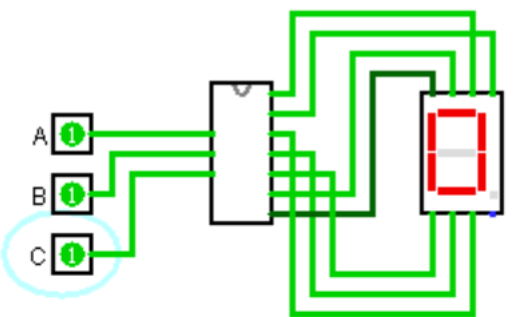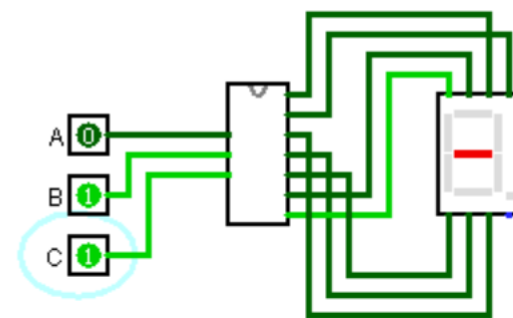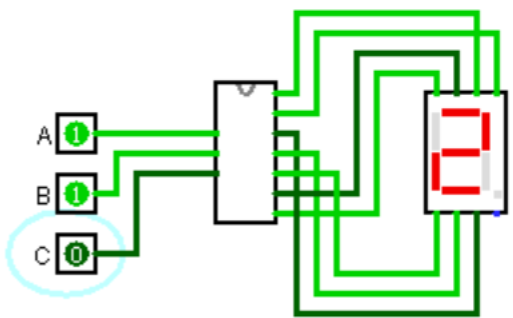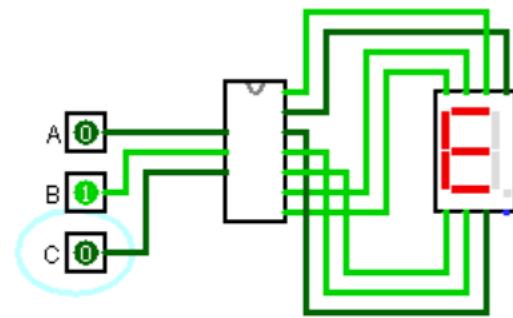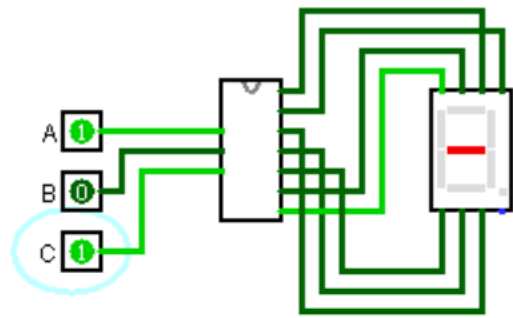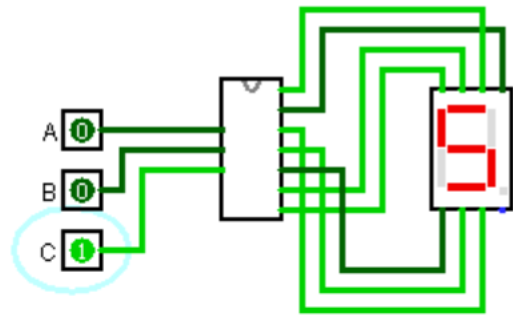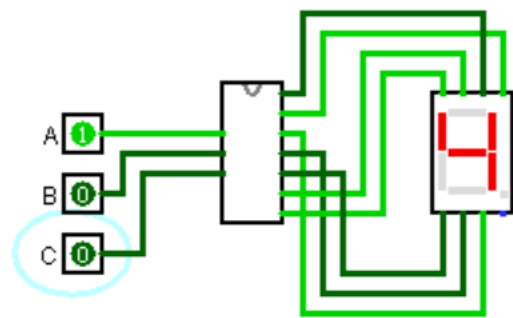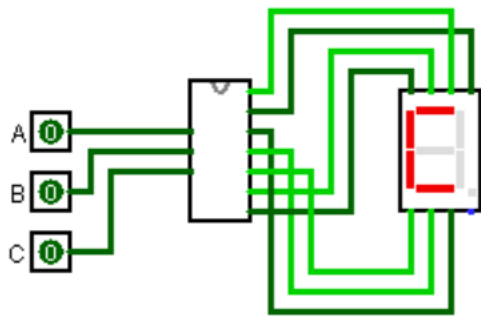
POS is done by Israt Jahan Meem  
ID: 2012036642











## Using NAND Gate Circuit

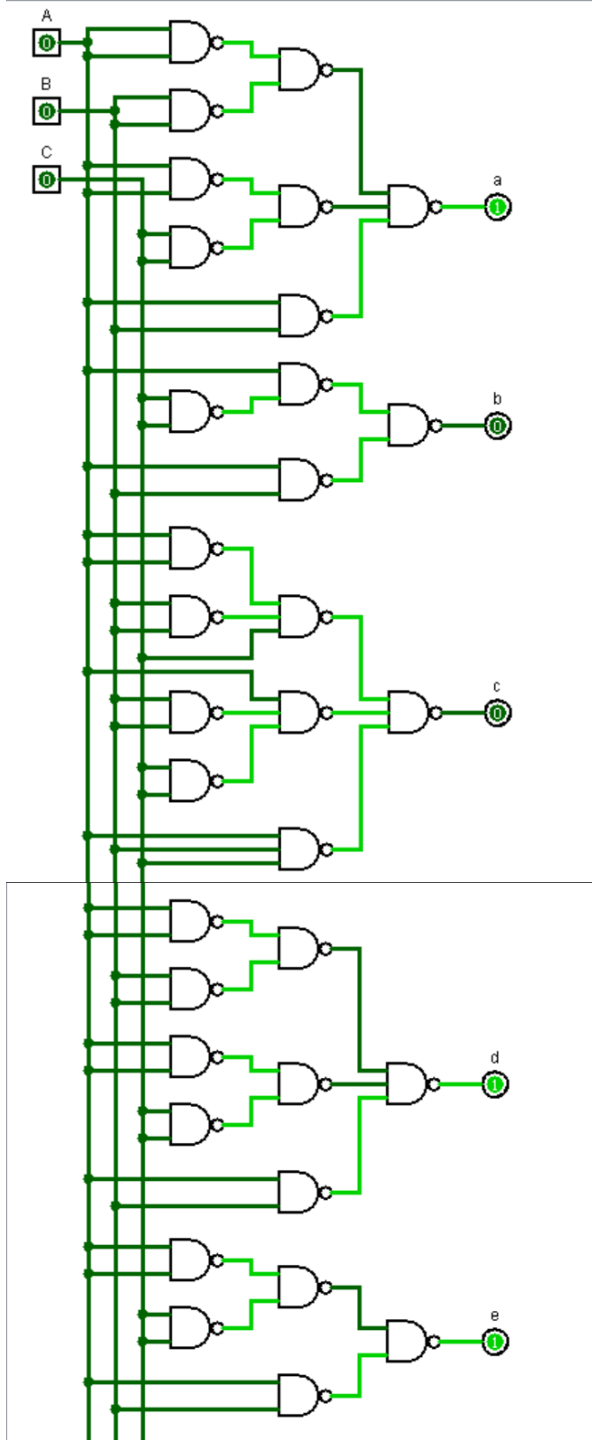


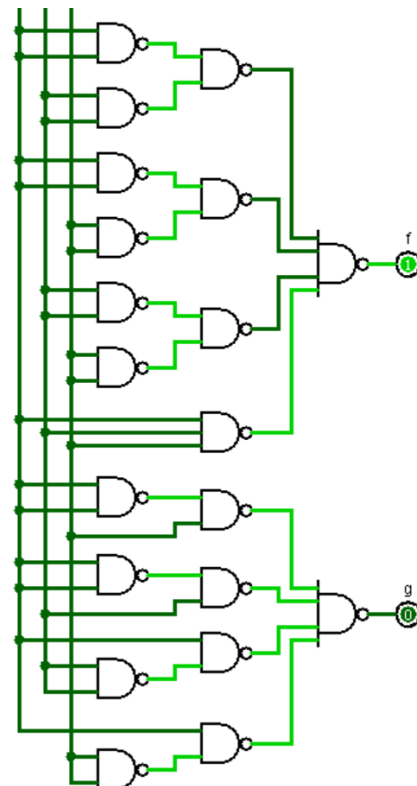NAND is done by Sabbir Hossain Saykot  
ID: 2014160042



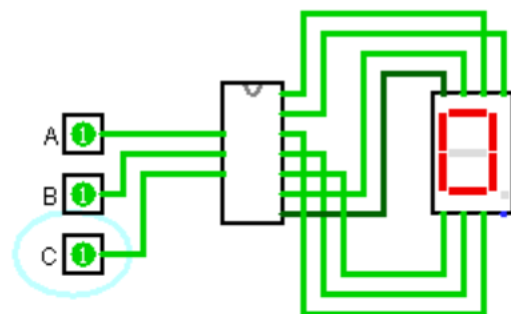
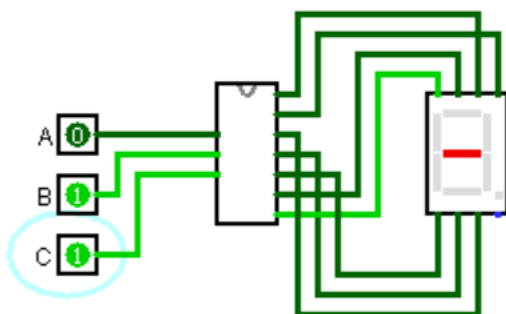
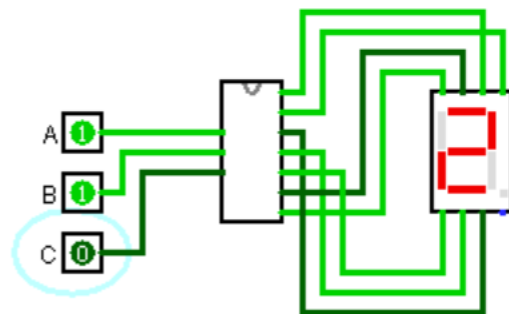
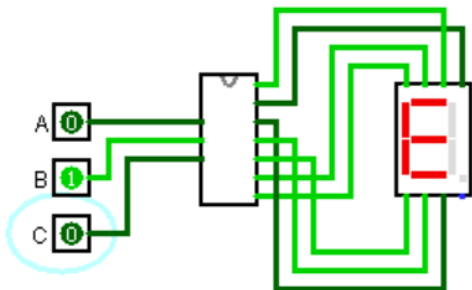
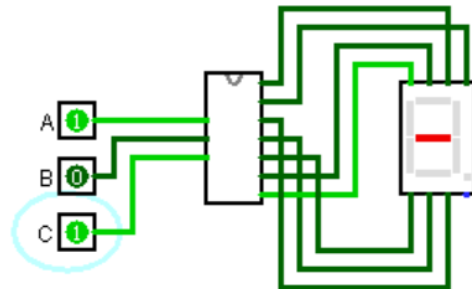
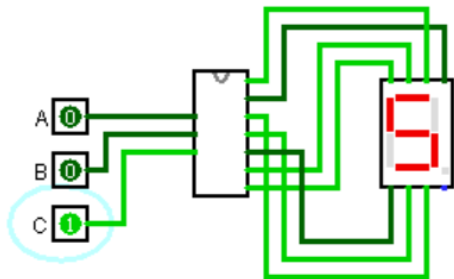
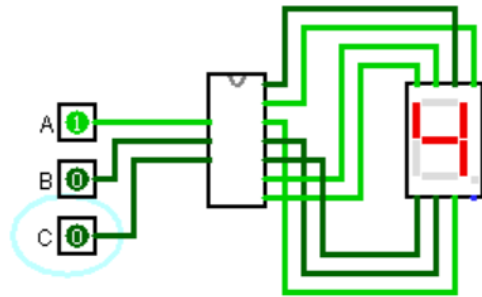
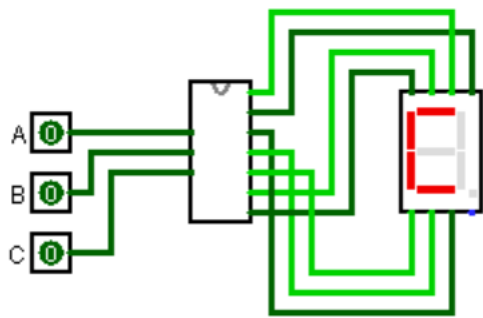


## Using NOR Gate Circuit






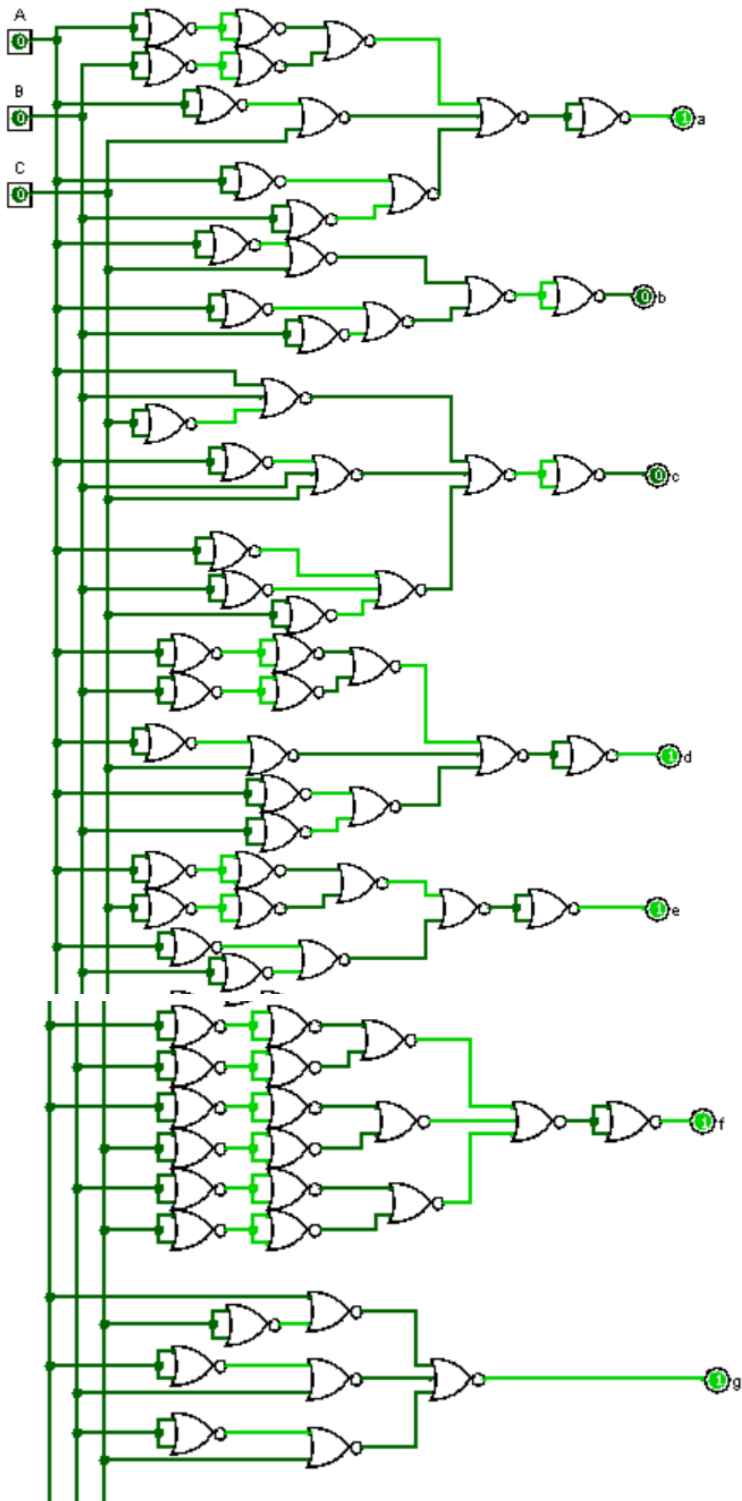


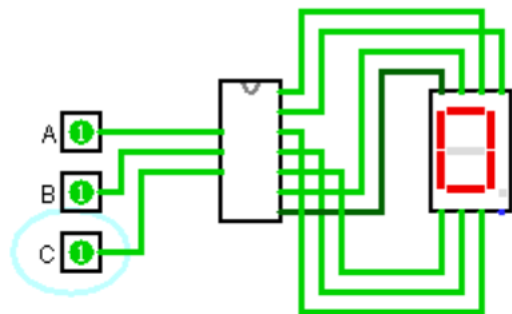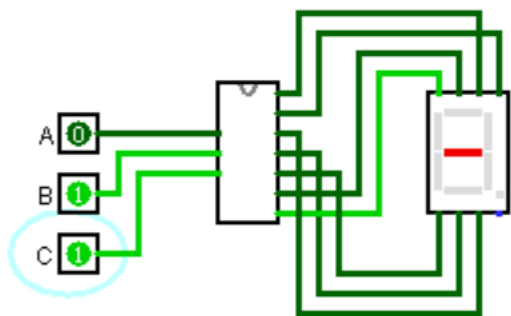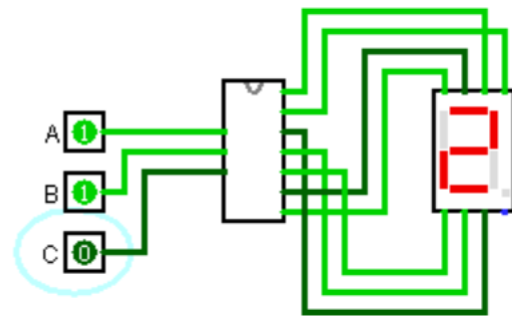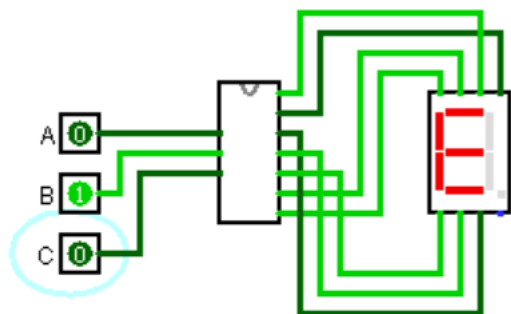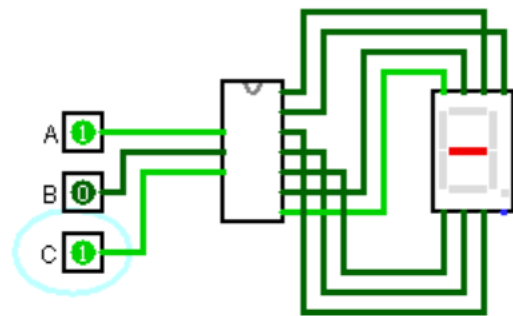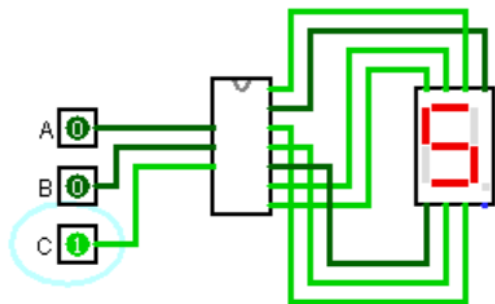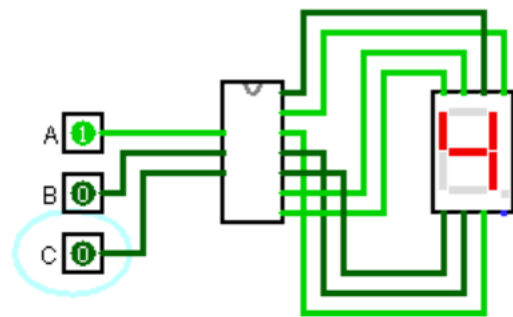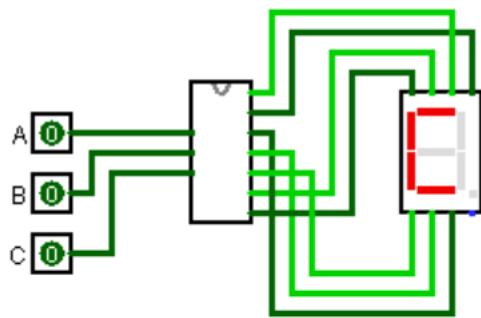
NOR is done by Rayan Ahmed.  
ID: 2013130642





## Using Multiplexer

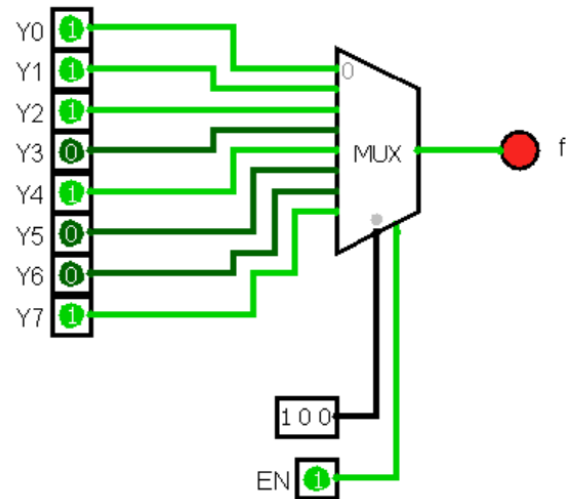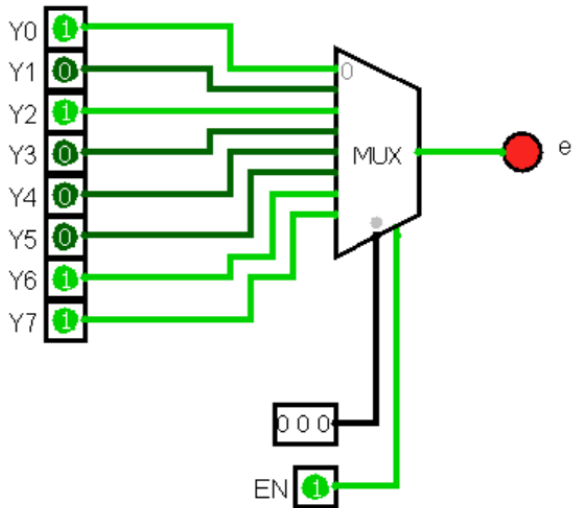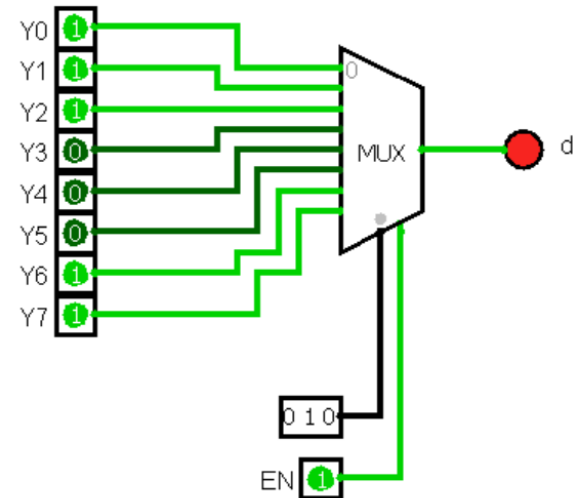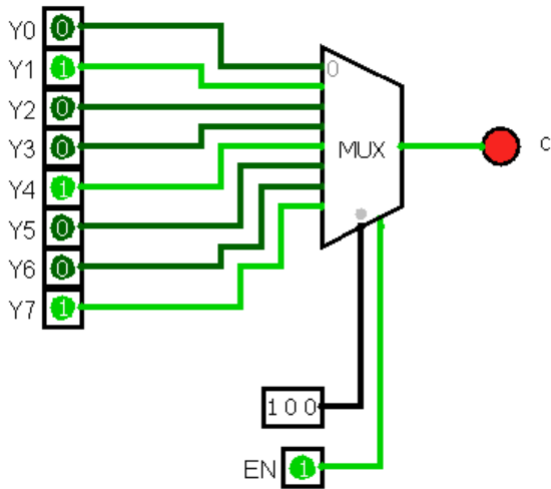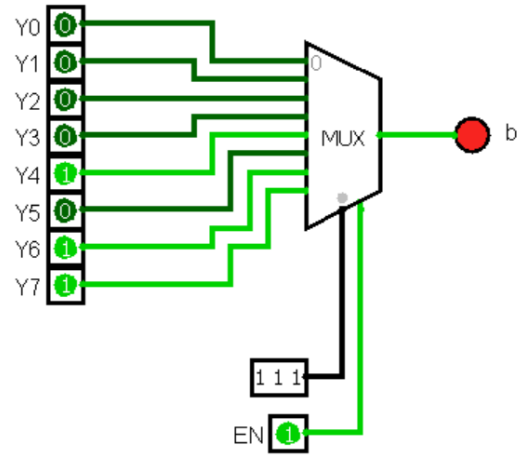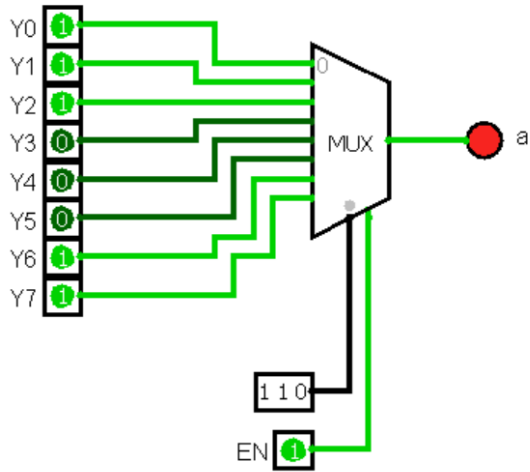

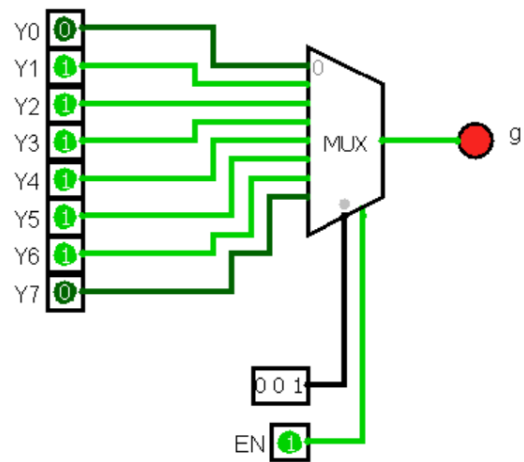

Multiplexer is done by Tanvir Rahman Navin.  
ID: 2012440642